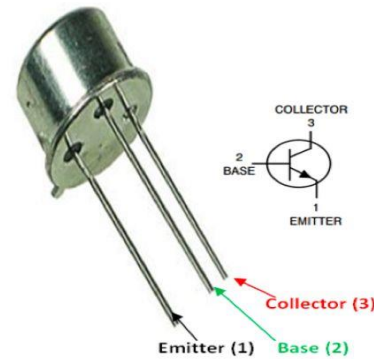


JUNCTION TRANSISTOR STRUCTURE & SURPRISING ACTION OF TRANSISTOR



BIPOLAR JUNCTION TRANSISTORS (BJTs)




Er. J. Sravankumar

Asst. Professor

Department of Basic Engineering and Applied Sciences
College of Agricultural Engineering and Technology(CAET),
Anand Agricultural University(AAU), Godhra



INTRODUCTION

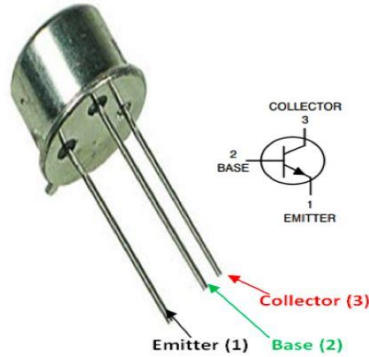

Invented in 1948

By


John Bardeen, Walter Brattain and William Shockley
@ Bell Laboratories in America

Revolutionized the electronics industry




JUNCTION TRANSISTOR STRUCTURE

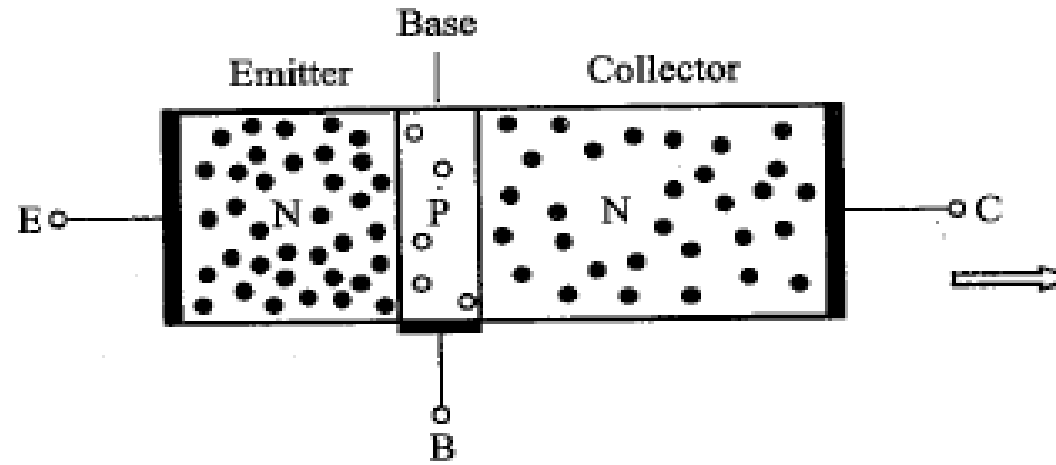Majority Charge Carriers: Electrons
Minority Charge Carriers: Holes




(a) NPN-type

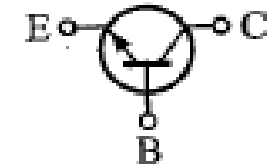


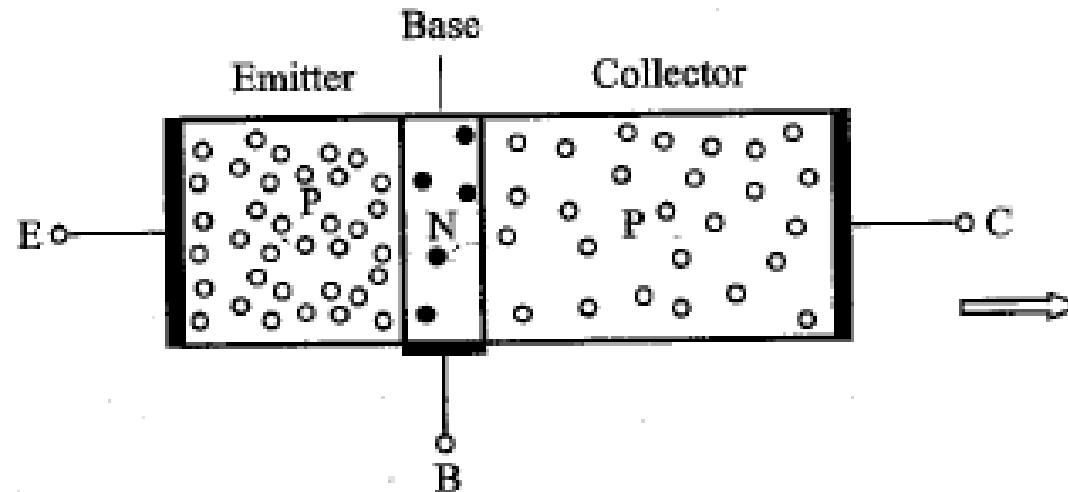(b) NPN-transistor symbol

Majority Charge Carriers: Holes
Minority Charge Carriers: Electrons



(c) PNP-type

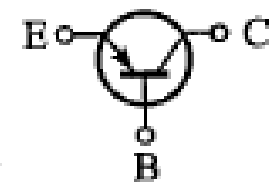

(d) PNP-transistor symbol



Transistor is basically a silicon or germanium crystal

THREE separate regions

NPN-type or PNP-type

Emitter : Heavily doped :emit or inject electrons (holes in case of PNP transistor) in to the base

Base : Lightly doped : passes most of these electrons(holes in PNP) from emitter on to collector

Collector : Moderately doped : collects electrons(holes in PNP) from base

A transistor has two PN-junctions

The junction between the emitter and the base and is called the **emitter-base junction or simply the *emitter junction***

The junction between the collector and the base and is called the **collector-base junction or simply the *collector junction***



THE SURPRISING ACTION OF A TRANSISTOR

junctions 2

emitter junction and
a collector junction

4

ways
of
biasing

Condition		Emitter Junction	Collector Junction	Region of operation
I	FR	Forward biased	Reverse biased	Active
II	FF	Forward biased	Forward biased	Saturation
III	RR	Reverse biased	Reverse biased	Cutoff
IV	RF	Reverse biased	Forward biased	Inverted



FR CONFIGURATION

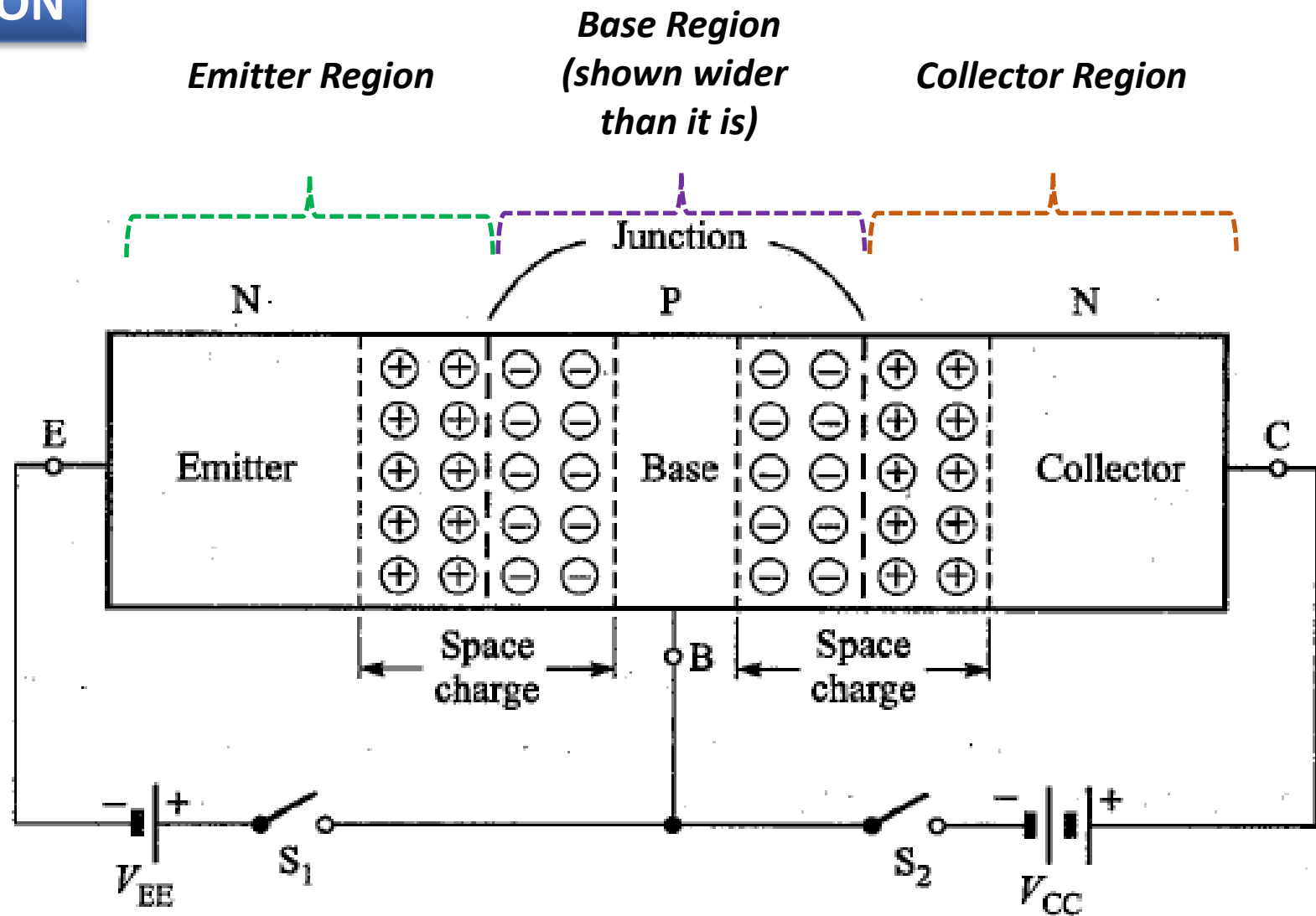


Fig : Biasing an NPN transistor for active operation




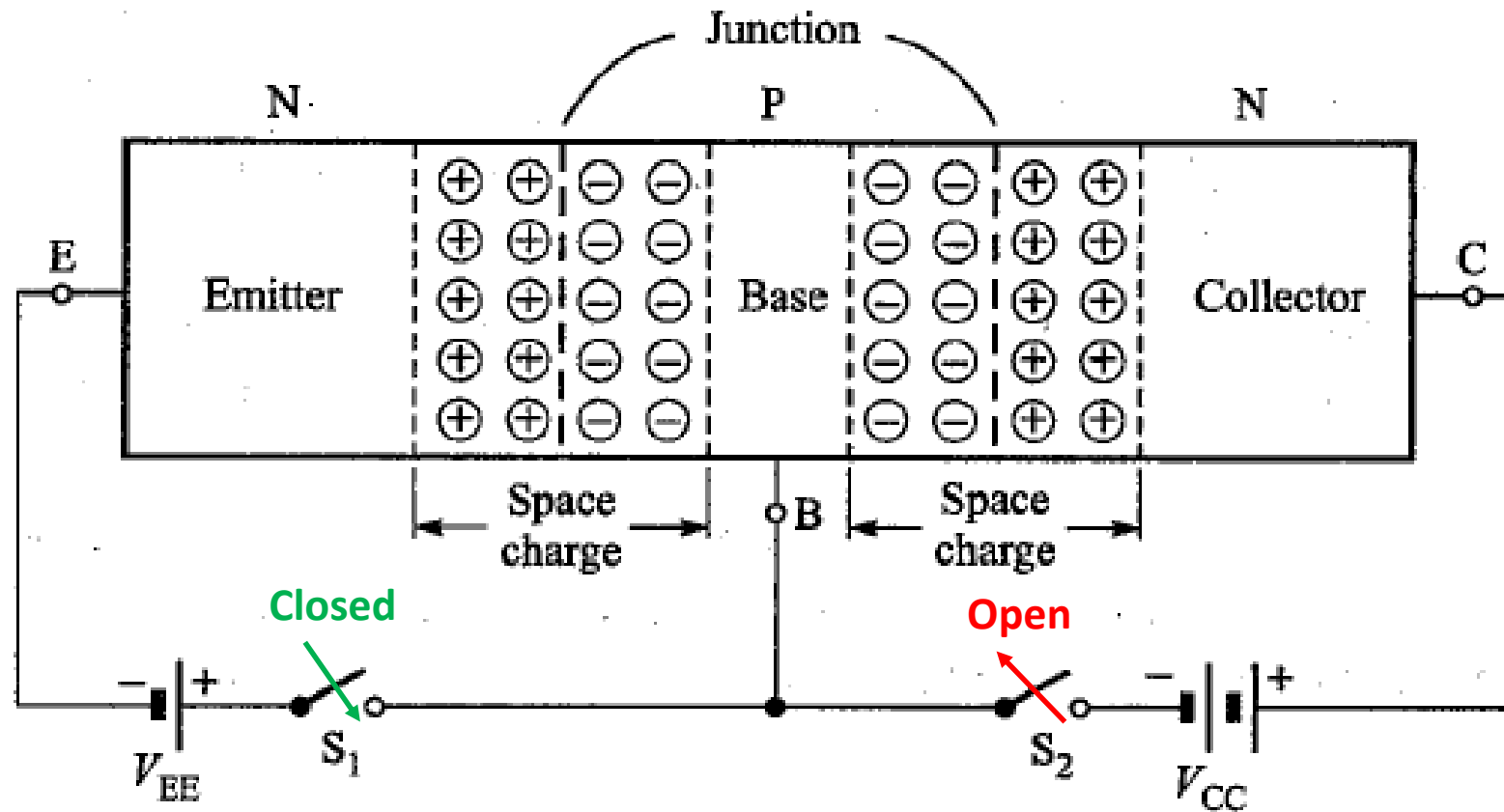


Fig : Biasing an NPN transistor for active operation

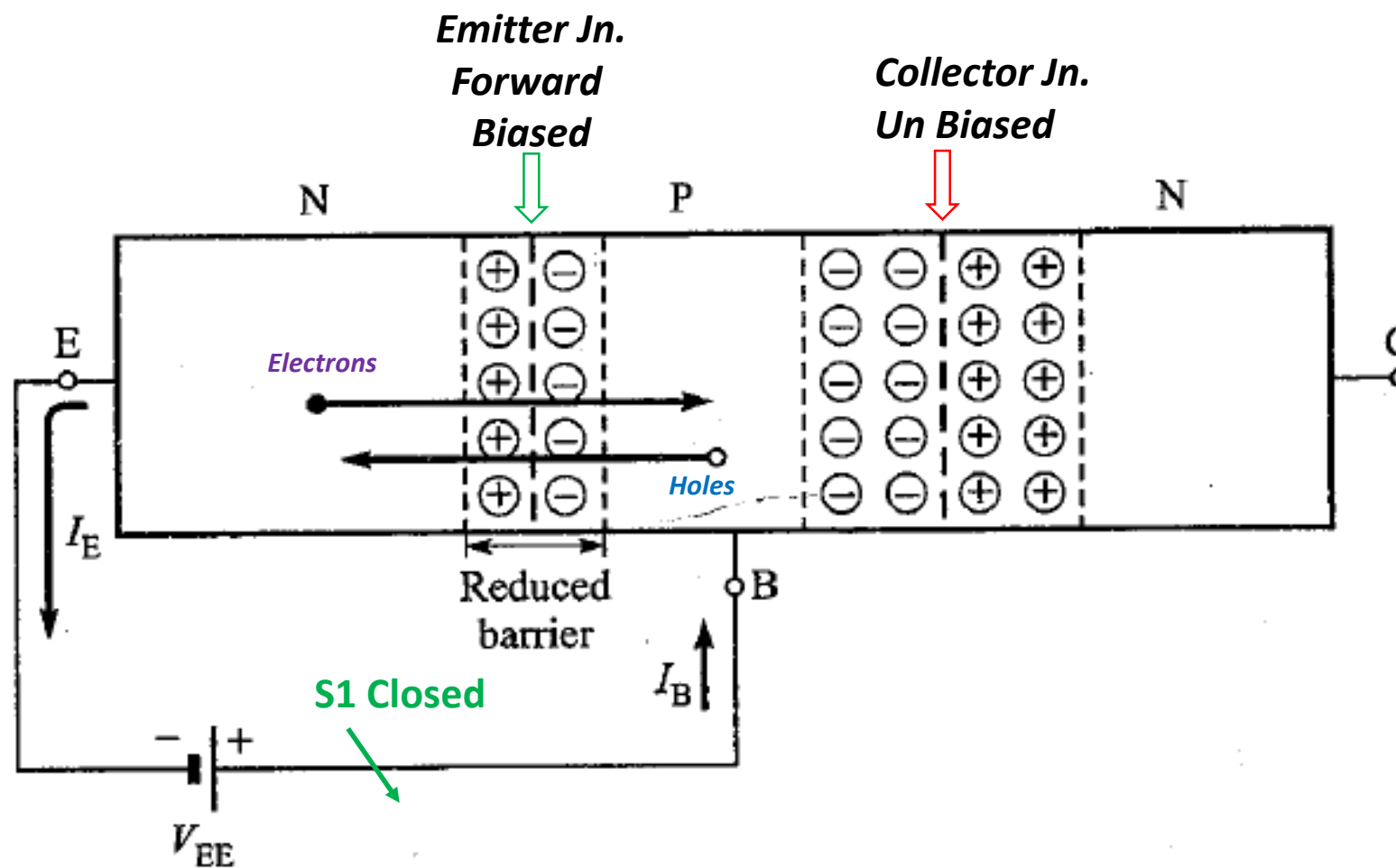



Total current flowing across the junction is sum of electron diffusion current and hole diffusion current


Base → Deliberately Doped → Few Holes → VERY LESS HOLE CURRENT

Emitter → Heavily Doped → Majority electron carriers → 99% ELECTRON CURRENT diffusing from emitter to base

Emitter currents (I_E) and Base currents (I_B) are quite large and equal ($I_E = I_B$)

Collector current (I_C) = 0



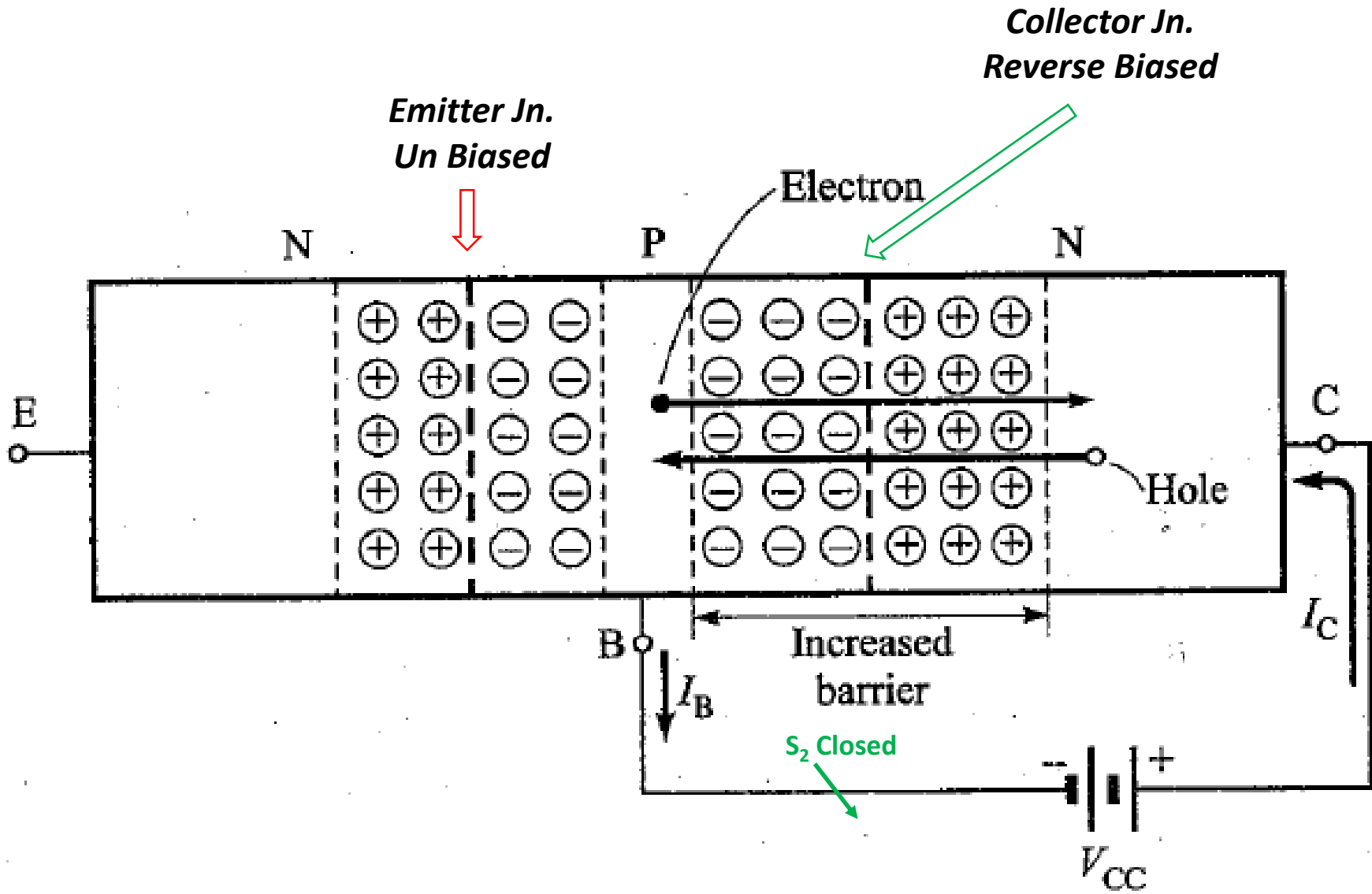



Very small current flows across this reverse-biased junction

The reverse leakage current (I_{CBO}) is due to the movement of minority carriers.

The current flows into the collector lead and out of the base lead.

There is no emitter current ($I_E = 0$).



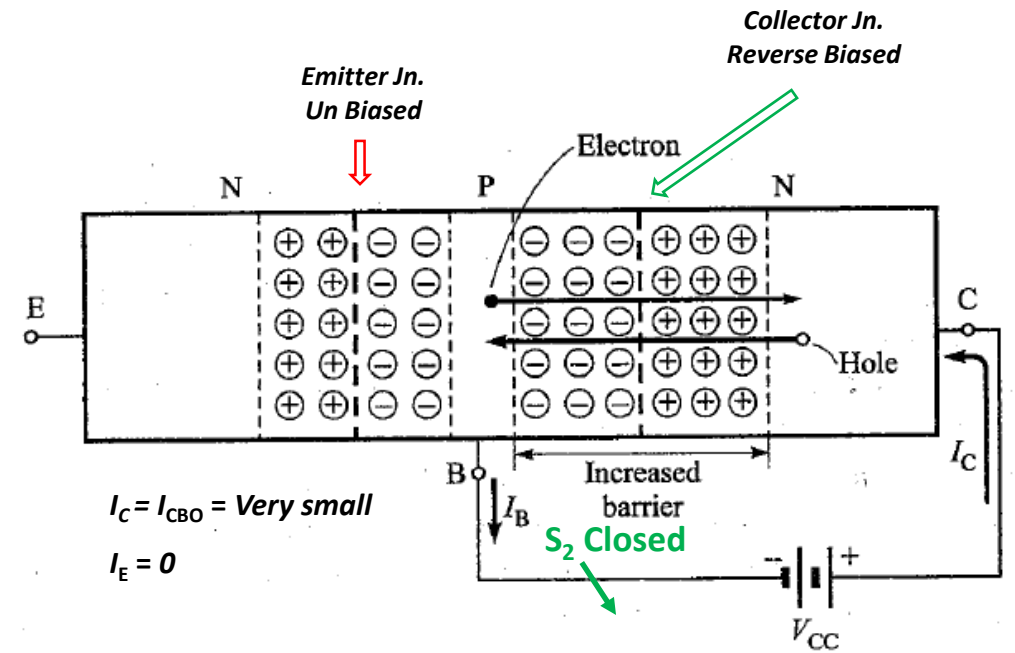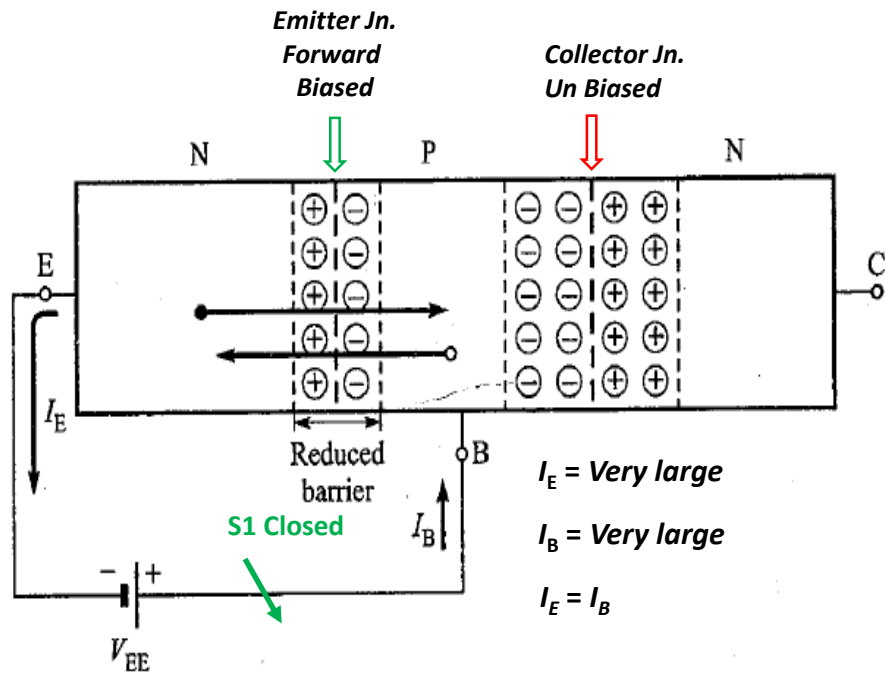


Expected

- $I_E = \text{Very large}$
- $I_B = \text{Very large}$
- $I_E = I_B$
- $I_C = I_{CBO} = \text{Very small}$

Actual

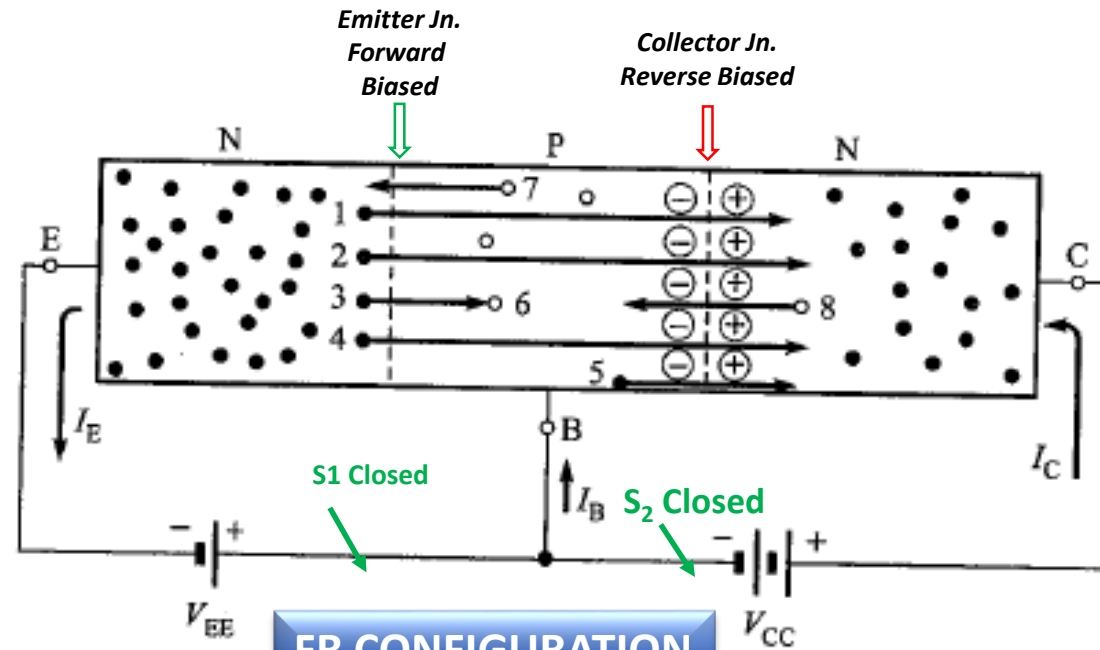- $I_E = \text{large (as expected)}$
- $I_B = \text{very small (surprising)}$
- $I_C = \text{large current (surprising)}$



FR CONFIGURATION



In the next section,
we shall investigate the reason
for I_C being large and I_B being
small.

