



BIPOLAR JUNCTION TRANSISTORS (BJTs)



Er. J. Sravankumar

THE SURPRISING ACTION OF A TRANSISTOR

junctions **2**

emitter junction and
a collector junction


4

ways
of
biasing

Condition		Emitter Junction	Collector Junction	Region of operation
I	FR	Forward biased	Reverse biased	Active
II	FF	Forward biased	Forward biased	Saturation
III	RR	Reverse biased	Reverse biased	Cutoff
IV	RF	Reverse biased	Forward biased	Inverted

- Electrons
- Holes

Condition		Emitter Junction	Collector Junction	Region of operation
I	FR	Forward biased	Reverse biased	Active

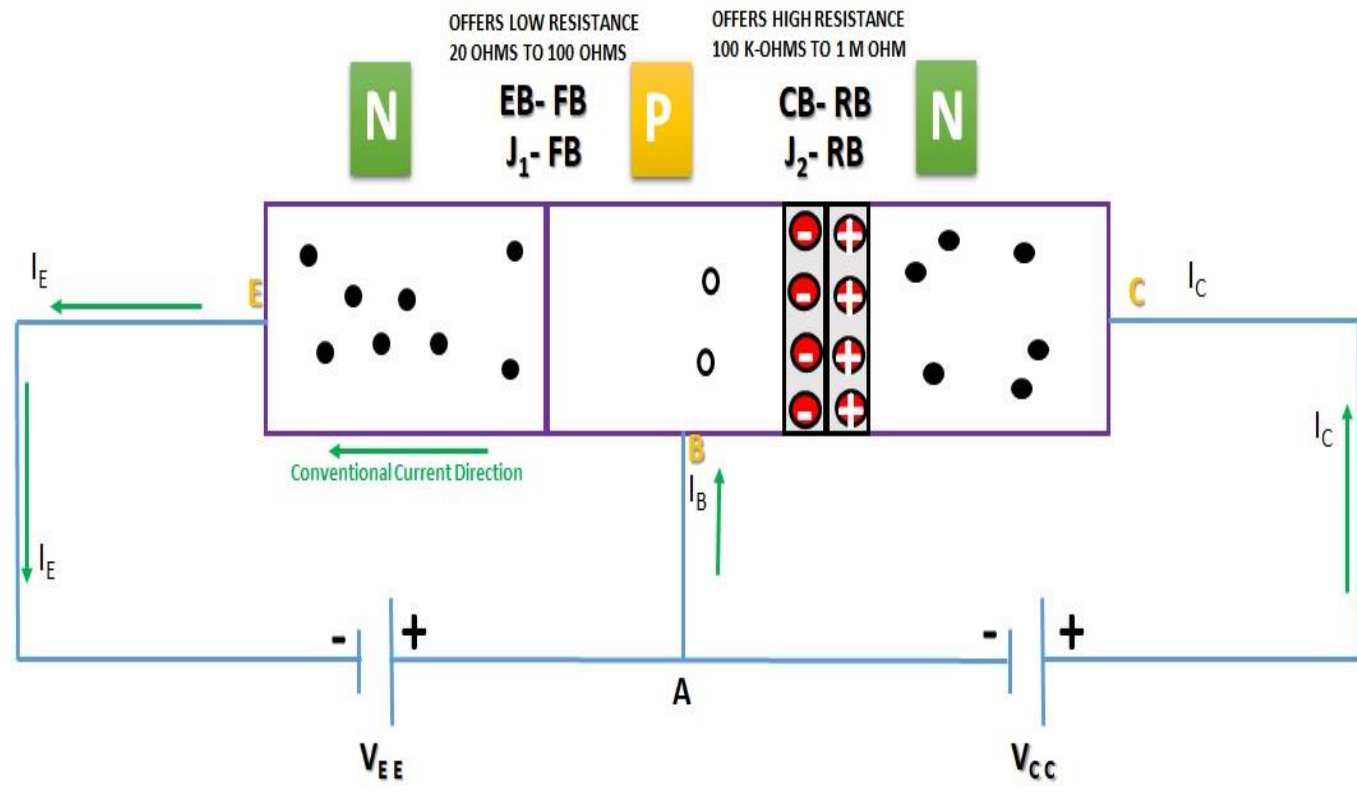

@ A: Applying KCL: $I_E = I_B + I_C$

Also : $I_C = \alpha_{dc} I_E + I_{CO}$

Where reverse leakage current, I_{CO} =very small and can be neglected

$$I_C = \alpha_{dc} I_E$$


$$\alpha_{dc} = \frac{I_C}{I_E}$$

$$0.95(\text{always}) < \alpha_{dc} = \frac{I_C}{I_E} < 1(\text{always})$$


- Electrons
- Holes

Two port network


Condition		Emitter Junction	Collector Junction	Region of operation
I	FR	Forward biased	Reverse biased	Active

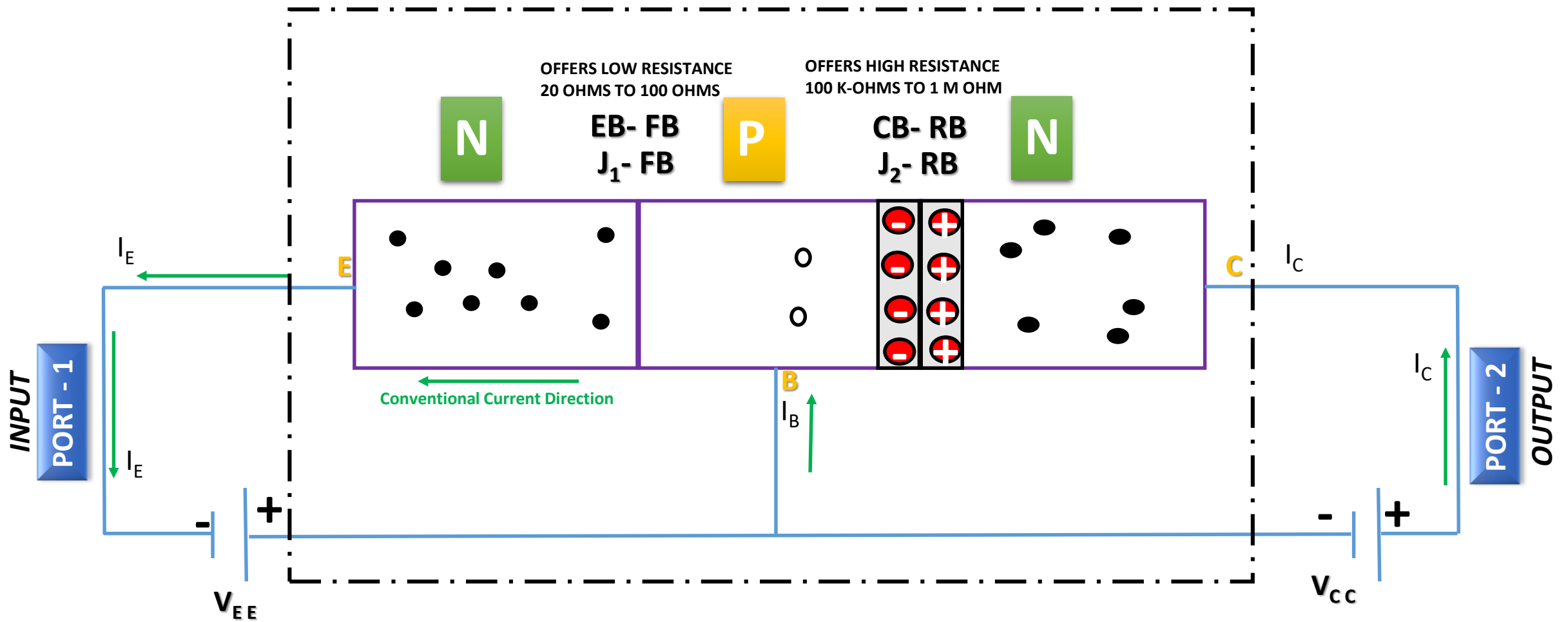

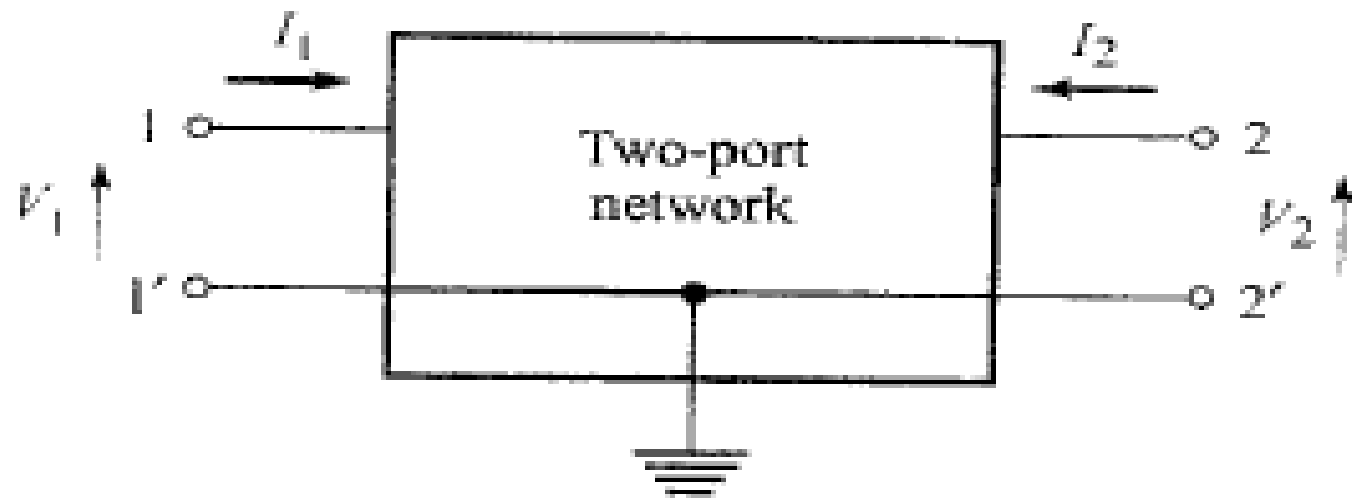
Transfers current signal from low resistance to high resistance
TRANSFER + RESISTOR = TRANSISTOR



(a) Two-port network

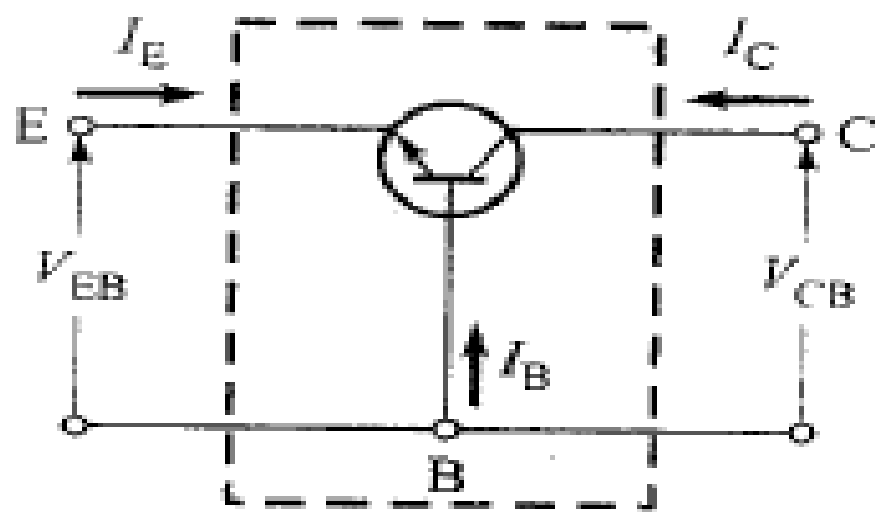


(b) NPN transistor

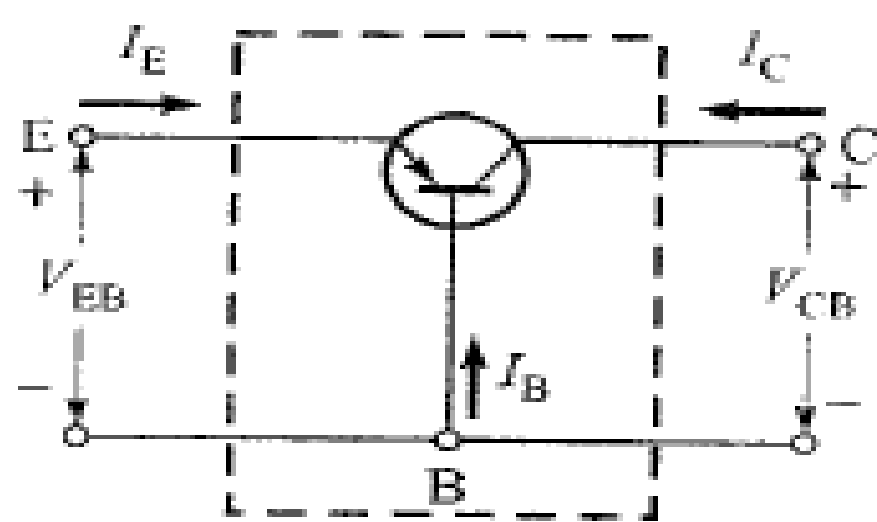

(c) PNP transistor

AMPLIFYING ACTION OF A TRANSISTOR

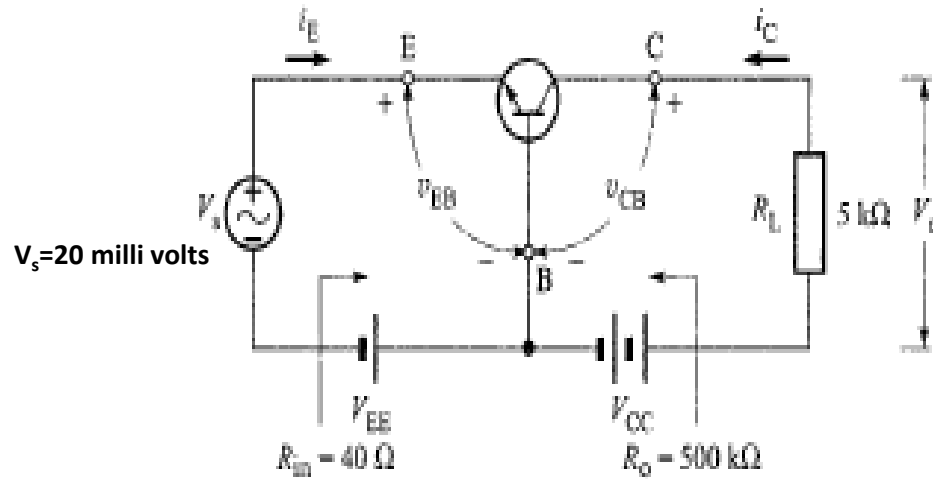

Input signal, $V_s = 20 \text{ m Volts}$

$$\text{Emitter current, } I_e = \frac{V_s}{R_{in}} = \frac{20 \times 10^{-3}}{40} = 0.5 \text{ mA}$$

Collector Current, $I_c \cong I_E = 0.5 \text{ mA}$

The effective value of the output signal voltage,

$$\begin{aligned} V_0 &= I_c \cdot R_L \\ &= (0.5 \times 10^{-3})(5 \times 10^3) = 2.5 \text{ volts} \end{aligned}$$

Condition	Emitter Junction	Collector Junction	Region of operation
I FR	Forward biased	Reverse biased	Active

$$\text{Voltage Amplification or voltage gain } (A_v) = \frac{V_0}{V_s} = \frac{2.5}{20 \times 10^{-3}} = 125$$