

HALF WAVE RECTIFIER (use of Diodes in Rectifiers)

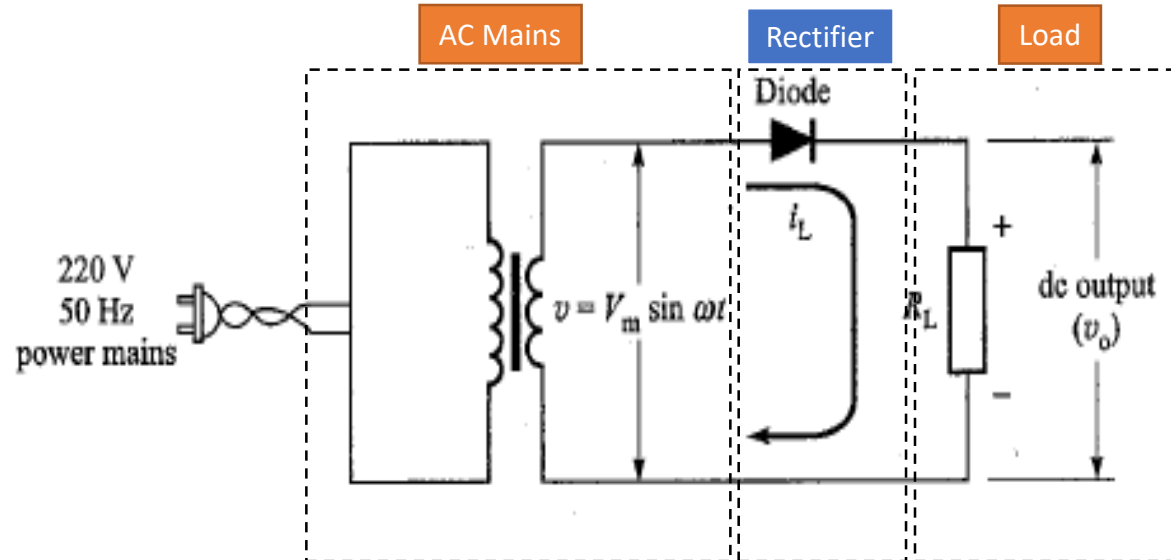


Fig : Half-wave rectifier circuit



Er. J. Sravankumar

Asst. Professor

Department of Basic Engineering and Applied Sciences
College of Agricultural Engineering and Technology(CAET),
Anand Agricultural University(AAU), Godhra

USE OF DIODES IN RECTIFIERS

Available Electrical Energy in
(alternating in nature(AC))

INDIA : 220Vrms@50Hz

US :110V @60Hz

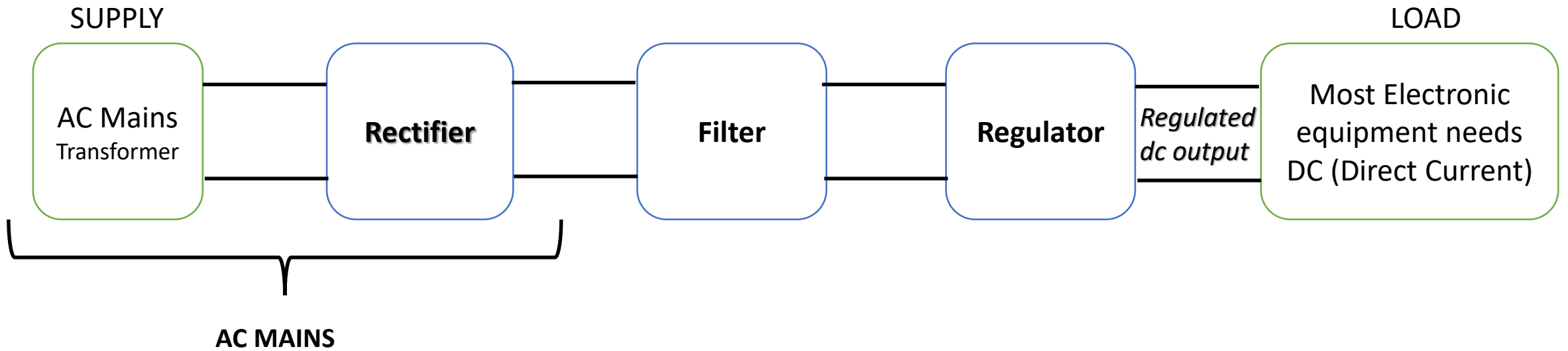
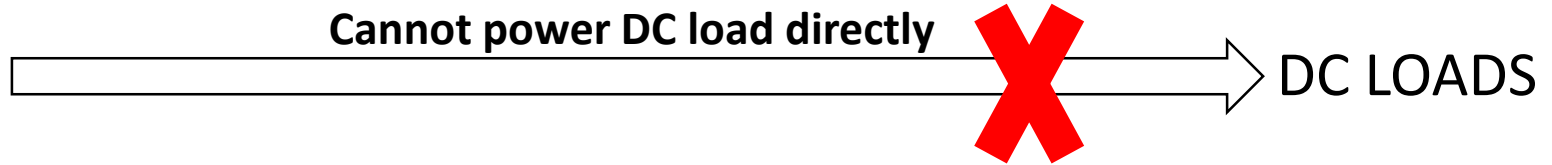


Fig : Block diagram of a power supply

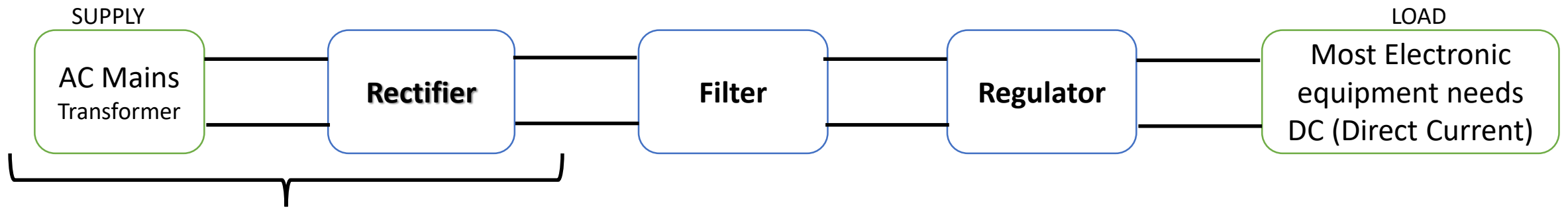


Fig : Block diagram of a power supply

AC MAINS

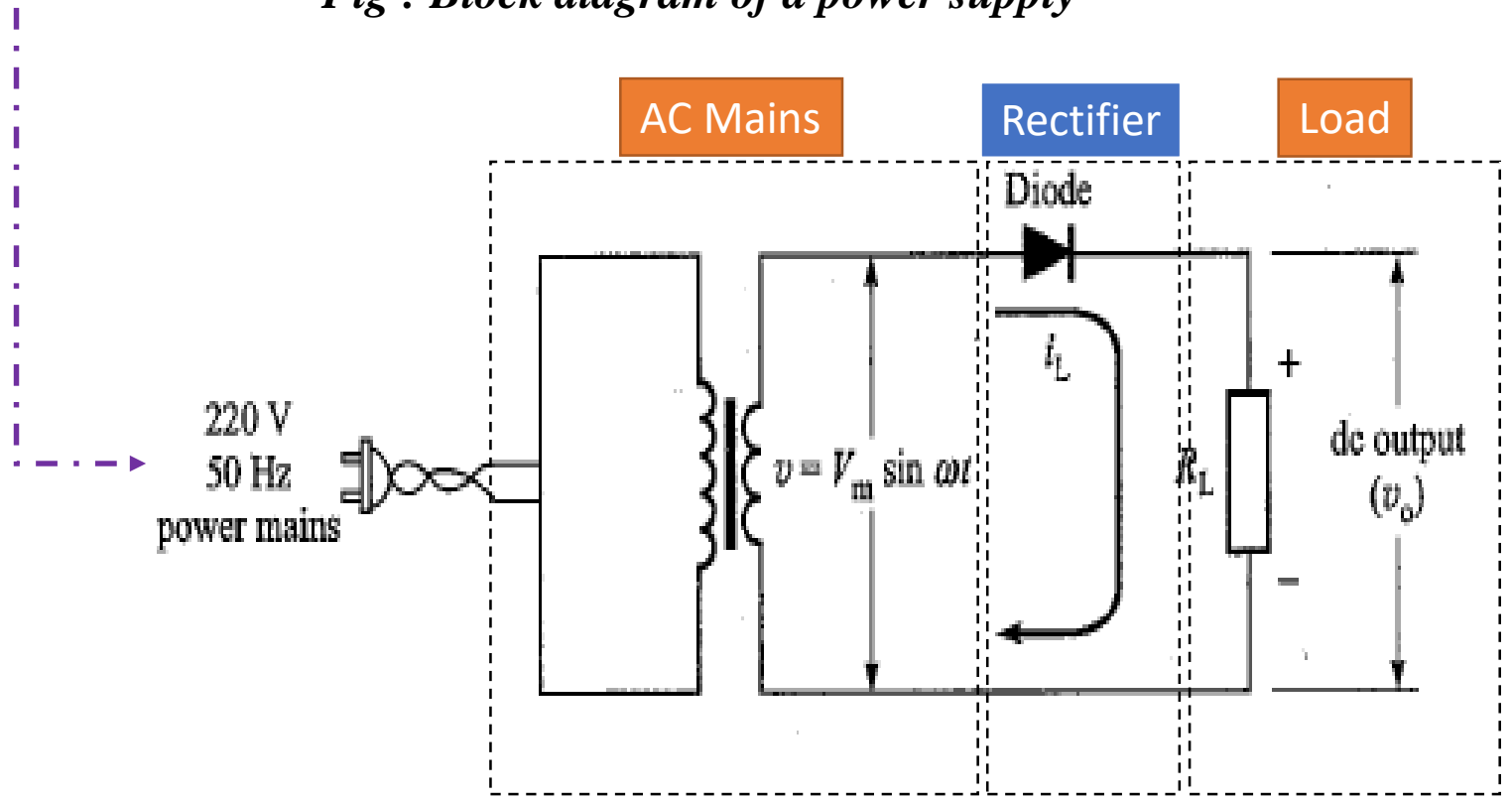


Fig : Half-wave rectifier circuit



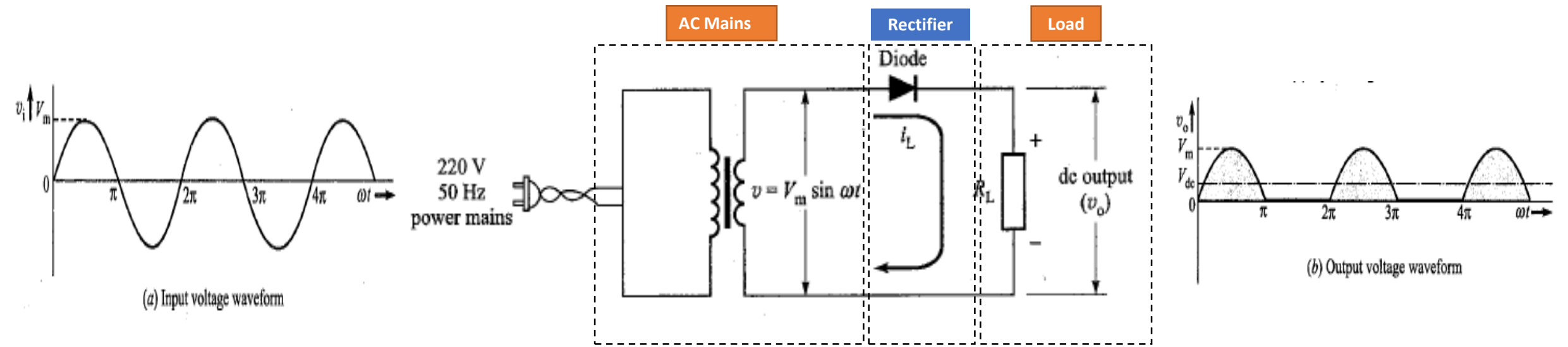




Fig : Half-wave rectifier circuit with input-output voltage waveforms

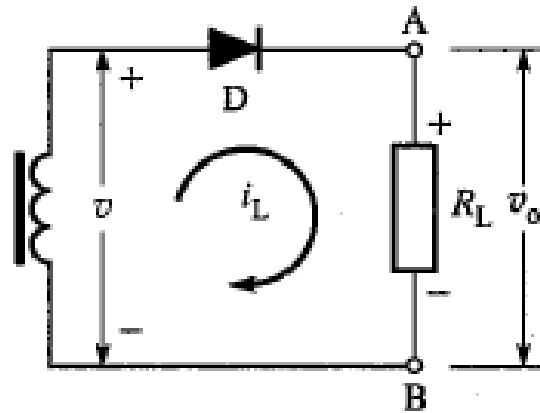



(a) During positive half-cycle

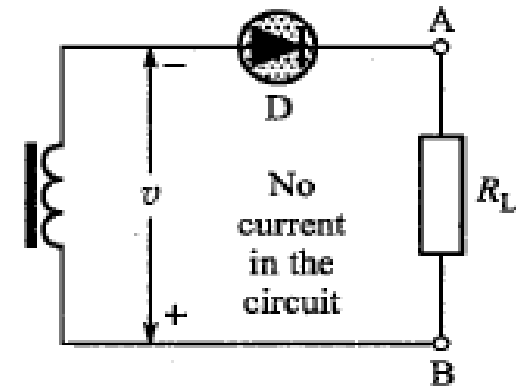

(b) During negative half-cycle

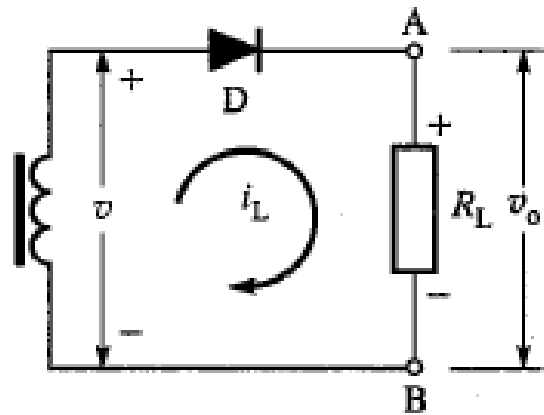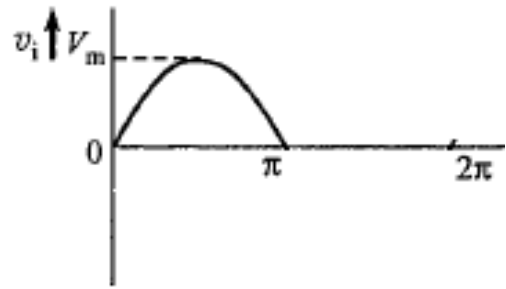

(a) During positive half-cycle

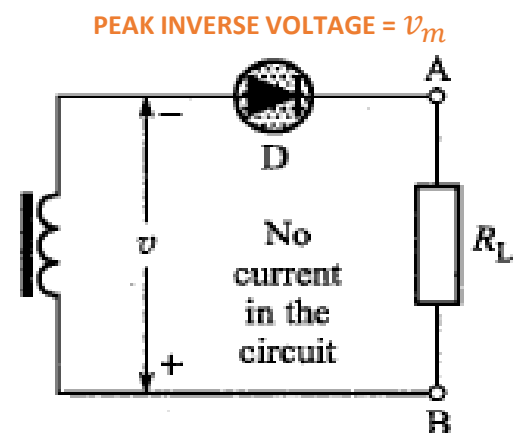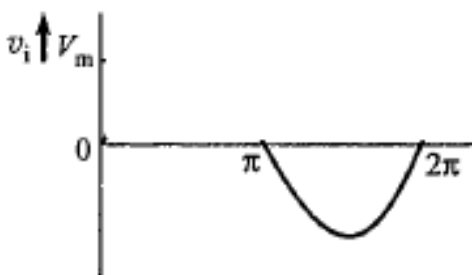

(b) During negative half-cycle

Contributes output between 0 to π

Contributes output between π to 2π


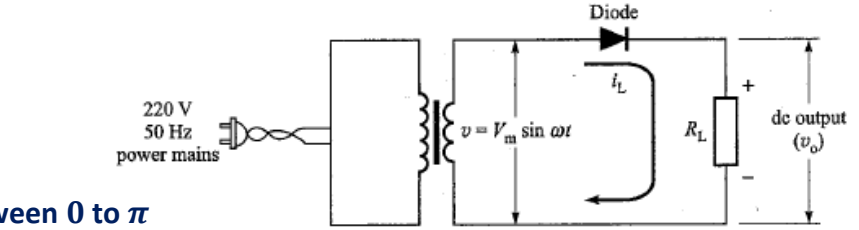


Fig : Half-wave rectifier circuit

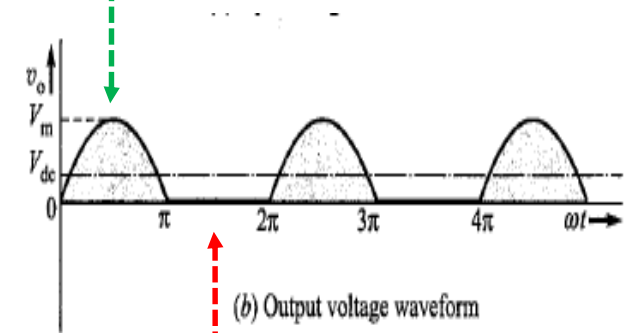

(b) Output voltage waveform



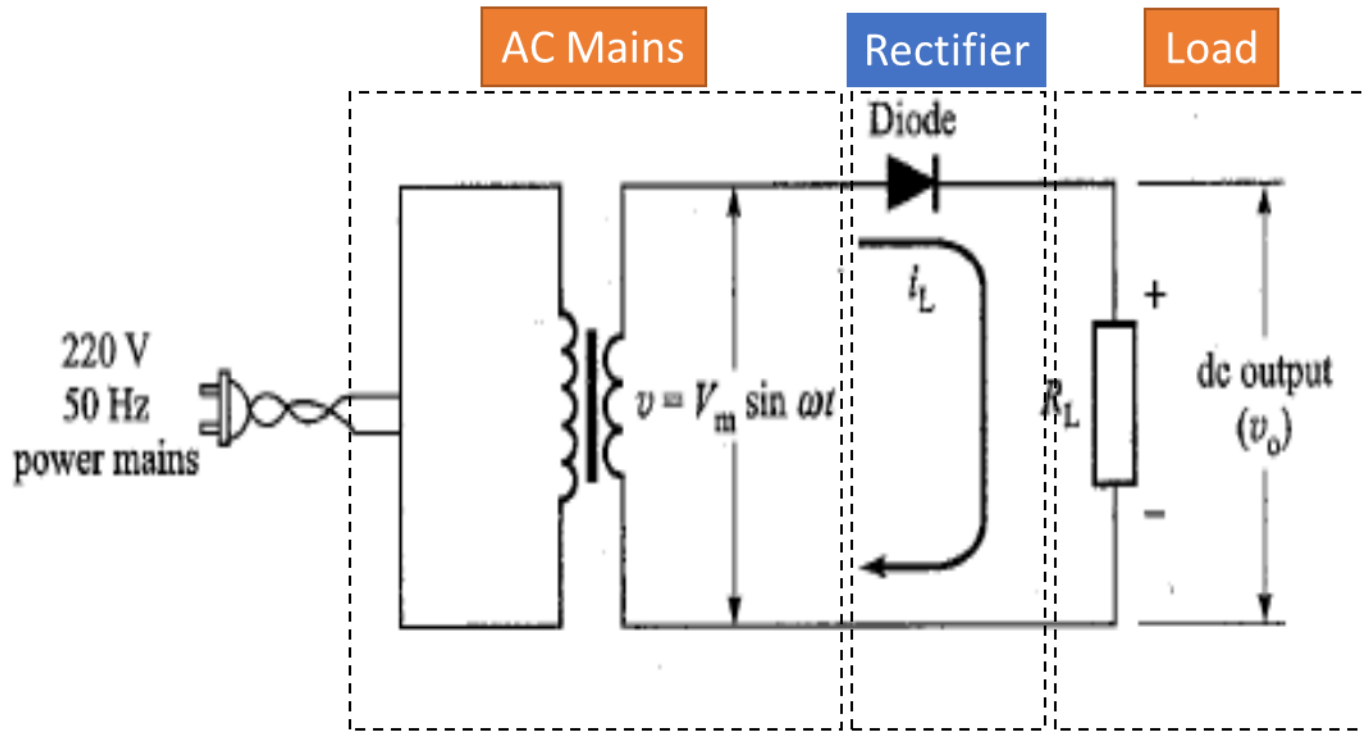


Fig : Half-wave rectifier circuit

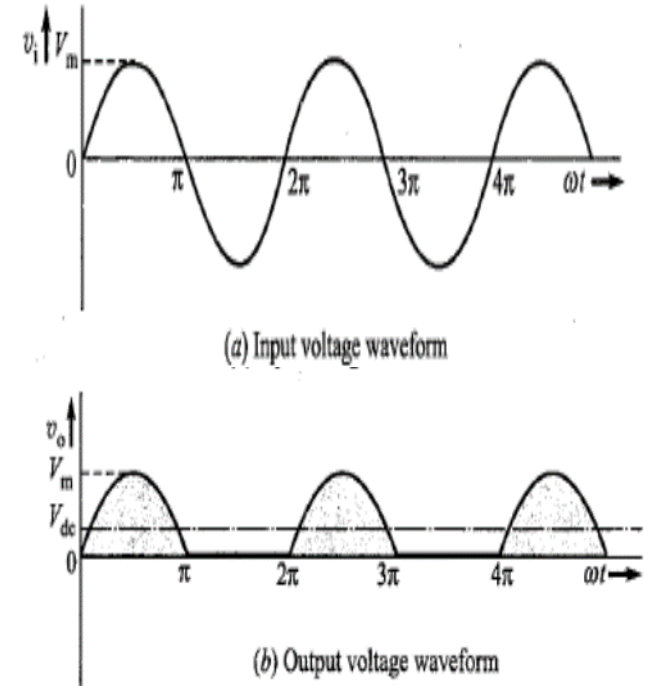

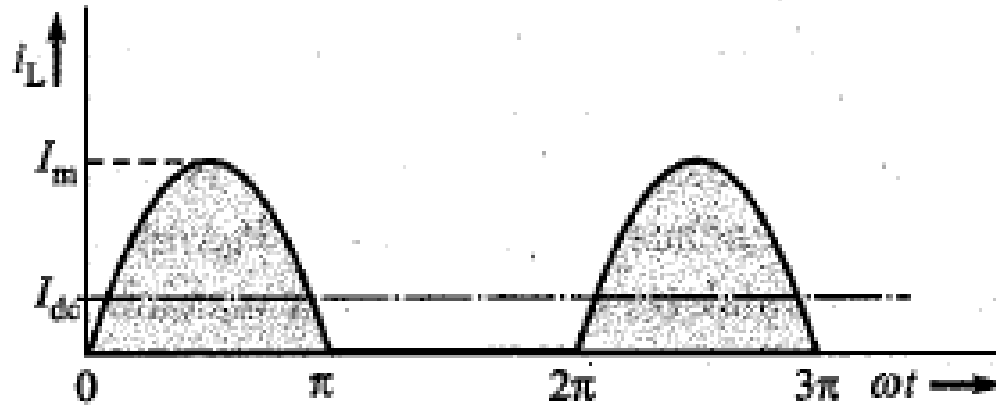

Waveform of the current flowing through load R_L in a half-wave rectifier

$$i_L = I_m \sin \omega t \text{ for } 0 \leq \omega t \leq \pi$$

$$i_L = 0 \text{ for } \pi \leq \omega t \leq 2\pi$$

Here I_m is the peak value of the load current i_L
&


Related to peak value of the voltage v_m

$$\text{as } I_m = \frac{v_m}{R_L + r_d}$$

Here, r_d is diode resistance

Output dc voltage: net area under the curve over one complete cycle(0 to 2 π) and then divide this area by base 2π

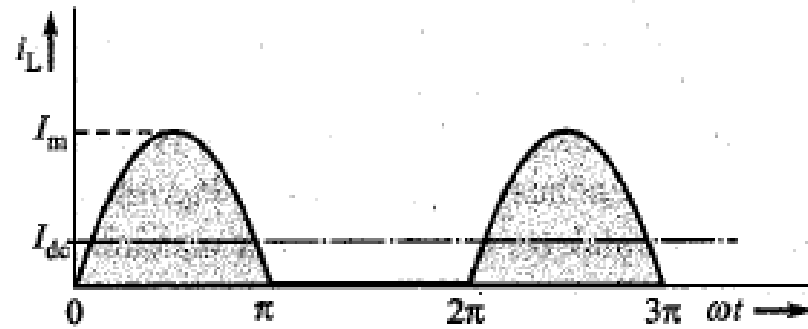Output dc voltage: net area under the curve over one complete cycle(0 to 2π) and then divide this area by base 2π



Waveform of the current flowing through load R_L in a half-wave rectifier

$$\text{Area} = \int_0^{2\pi} i_L d(\omega t)$$

$$= \int_0^{\pi} i_L d(\omega t) + \int_{\pi}^{2\pi} i_L d(\omega t)$$

$$= \int_0^{\pi} I_m \sin \omega t d(\omega t) + \int_{\pi}^{2\pi} 0 d(\omega t)$$

$$= I_m [-\cos \omega t]_0^{\pi} + 0$$

$$= I_m [-\cos \pi - (-\cos 0)]$$

$$= 2I_m$$

Average value of the load current is then

$$I_{avg} = I_{dc} = \frac{\text{Area}}{\text{Base}} = \frac{2I_m}{2\pi}$$

or

$$I_{dc} = \frac{I_m}{\pi}$$

Peak value of the load current I_m as $I_m = \frac{v_m}{R_L + r_d}$


Average value of the load current is then $I_{dc} = \frac{I_m}{\pi}$

The dc voltage developed across the load R_L is $V_{dc} = I_{dc} \times R_L = \frac{I_m}{\pi} R_L$


The dc voltage across the load resistor R_L can now be written with the help of I_m

$$V_{dc} = \frac{V_m}{\pi(R_L + r_d)} R_L = \frac{V_m}{\pi(1 + (\frac{r_d}{R_L}))}$$
$$\approx \frac{V_m}{\pi} \text{ (if } r_d \ll R_L)$$

SUMMARY

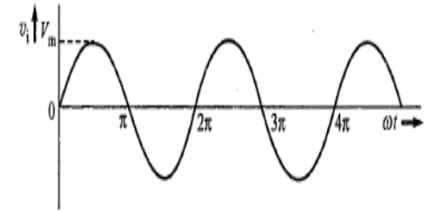

(a) Input voltage waveform

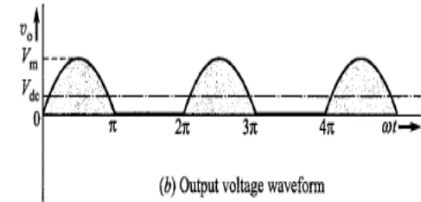

(b) Output voltage waveform

PEAK INVERSE VOLTAGE = v_m

$$I_m = \frac{v_m}{R_L + r_d}$$

$$I_{dc} = \frac{I_m}{\pi}$$

$$V_{dc} \approx \frac{V_m}{\pi} \text{ (if } r_d \ll R_L)$$